

GLOBAL ACADEMY OF TECHNOLOGY

(Autonomous Institution, Affiliated to VTU)

SEE MODEL QUESTION PAPER-I

UG

First Semester B.E. Degree Examination, April - 2021

Elements of Electronics Engineering

Time: 3 hrs.

Course Code: 20ELN16

Max. Marks: 100

Note: Answer any Five full questions, choosing ONE full question from each module.

Q. No.		MODULE - 1	Marks
1	a.	Explain the operation of a PN Junction diode under forward and reverse biased conditions with the help of VI characteristics.	8
	b.	Discuss the working of Half wave rectifier with circuit diagram and waveforms. Show that efficiency of half wave rectifier is 40.6 %.	7
	c.	Design Zener voltage regulator for the following specifications: Input Voltage= $10V \pm 20\%$, Output Voltage= 5V, $I_L = 20mA$, $I_Z \text{ min} = 5mA$ and $I_Z \text{ max} = 80mA$.	5
		OR	
2	a.	Discuss DC load line of a PN Junction diode.	6
	b.	A Half wave rectifier uses a transformer with turns ratio 2:1, the load resistance is 500Ω If the primary voltage is 240 V. Calculate peak inverse voltage and Dc Voltage	7
	c.	What is the need for a capacitive filter? Explain Full wave rectifier with capacitor filter.	7
		MODULE - 2	
3	a.	Explain the working and frequency response of an RC- Coupled amplifier.	7
	b.	Determine the dc bias voltage V_{CE} and the current I_c for the voltage divider configuration of Figure 3(b).	6
	c.	Discuss the working principles of RC- phase shift oscillator using BJT.	7
		OR	
4	a.	Determine R_B and R_C for the transistor inverter shown in Fig. 4(a) if $I_{C\text{sat}} = 10mA$	7

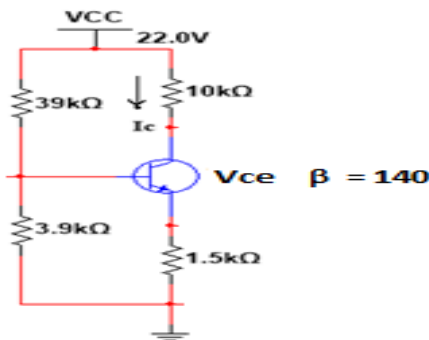
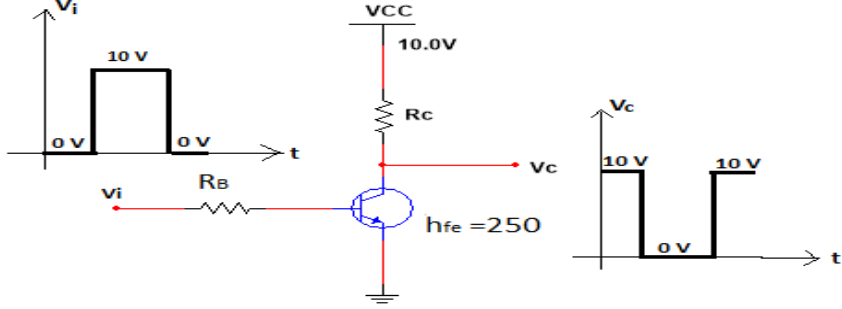
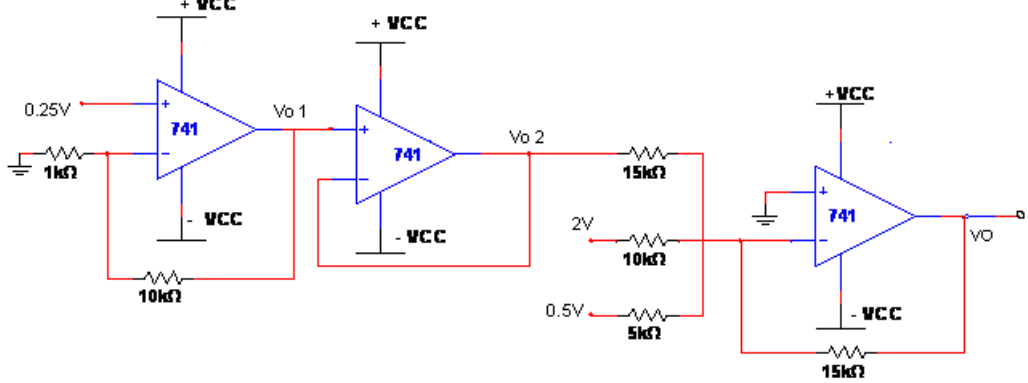


Fig. 3(b)

b	 <p style="text-align: right;">Fig. 4(a).</p>	6
c	<p>Explain Colpitts oscillator with circuit diagram and write the expression for the frequency of oscillation.</p> <p>Explain the working of fixed bias circuit and also obtain the expressions for I_B and V_{CE}.</p>	7

MODULE - 3

5	<p>a. Obtain an expression for the output voltage of an Inverting Amplifier using Op-amp and find the output voltage of a inverting amplifier with $V_{in} = 2\text{ V}$, $R_f = 500\text{ k}\Omega$ and $R_1 = 100\text{ k}\Omega$.</p> <p>b. Find the output voltage for the circuit shown in Fig. 5 (b).</p>  <p style="text-align: center;">Fig. 5 (b)</p> <p>c. Define the following terms with respect to Op-Amp and mention the typical values for IC 741 Op-Amp (i) CMRR (ii) Slew rate (iii) Input Bias Current (iv) Supply Voltage Rejection Ratio.</p>	5 4 8
---	---	---------------------

OR

6	<p>a. Explain the working principle of Inverting Schmitt Trigger with input and output waveforms.</p> <p>b. Design an adder circuit using Op-amp to obtain an output voltage of $V_0 = -[2V_1 + 3V_2 + 5V_3]$. Assume $R_f = 10\text{ k}\Omega$.</p> <p>c. Explain zero crossing detector using Op-amp and sketch the input and output waveforms</p>	7 7 6
---	--	-------------

MODULE - 4

7	<p>a. Perform the following operations:</p> <p>i) $(BCDE)_{16} \rightarrow (?)_2 \rightarrow (?)_{10}$</p> <p>ii) $(526.44)_{10} \rightarrow (?)_2 \rightarrow (?)_{16}$</p> <p>iii) $(10111101.0101)_2 \rightarrow (?)_{10} \rightarrow (?)_{16}$</p> <p>b. Deduce a Full adder using two half adders and write the truth table and logical expressions.</p> <p>c. Explain the working of an SR flip-flop with logic diagram and truth table.</p>	6 7 7
---	---	---------------------

		OR	
8	a.	Perform 1's and 2's Complement Subtraction for $(28)_{10} - (47)_{10}$.	5
	b.	Implement 4:1 Multiplexer using logic gates.	5
	c.	Explain the working of a JK flip-flop with help of Truth table.	5
	d.	List the Comparison between Combinational and Sequential logic Circuits.	5
		MODULE - 5	
9	a.	What is amplitude modulation? Deduce an expression for transmitted power in terms of carrier power.	7
	b.	What is modulation and explain the need for modulation.	6
	c.	A carrier of 1 MHz with 400 watts of its power is amplitude modulated with a sinusoidal signal of 2500 Hz. The depth of modulation is 75%. Calculate the sideband frequencies, the band width, the power in the side bands and the total power in the modulated wave.	7
		OR	
10	a.	Explain the block diagram of basic Communication System.	7
	b.	Discuss different types of Electronic Communication.	7
	c.	A 100 MHz carrier wave is frequency modulated by a 10Khz sinusoidal modulating signals. If the maximum frequency deviation is 50KHz. find the modulation index.	6