

GLOBAL ACADEMY OF TECHNOLOGY

(Autonomous Institution, Affiliated to VTU)

SEE MODEL QUESTION PAPER-2

UG

First Semester B.E. Degree Examination, April - 2021

Elements of Electronics Engineering

Time: 3 hrs.

Course Code: 20ELN16

Max. Marks: 100

Note: answer any Five full questions, choosing ONE full question from each module.

MODULE - 1			Marks
1	a.	Discuss the working of Full wave Bridge rectifier with circuit diagram and waveforms. Show that efficiency 81.2 %.	8
	b.	A full wave rectifier has a load of $1k\Omega$. The ac voltage applied to the diode is $200V-0V-200V$. If diode resistance is neglected, calculate (i) average dc current and (ii) average dc voltage.	8
	c.	Design a Zener voltage regulator to meet the following specifications: Output voltage = 5 V load current = 10 mA Zener wattage = 100 mW input voltage = $10 V \pm 2V$	4
OR			
2	a.	Discuss how Zener diode can be used for voltage regulation.	6
	b.	A full wave bridge rectifier with an input of 100 V (rms) feeds a load of $1 k\Omega$. $V_T = 0.7 V$ If the diodes employed are of silicon, what is the dc voltage across the load and determine the PIV rating of each diode.	7
	c.	Discuss the different types of Diode approximations.	7
MODULE - 2			
3	a.	Explain how transistor can be used as a Switch.	7
	b.	A voltage divider bias circuit has $V_{CC} = 15V$, $R_C = 2.7k\Omega$, $R_E = 2.2k\Omega$, $R_1 = 22k\Omega$, $R_2 = 12k\Omega$ and $h_{fe} = 50$. Calculate V_E , V_C , I_C and V_{CE} , draw the DC load line, and mark the Q-point assume $V_{BE} = 0.7V$.	6
	c.	Discuss working principles of Crystal Oscillator using BJT.	7
OR			
4	a.	Explain the operation of Hartlet oscillator with circuit diagram and write the expression for the frequency of oscillation.	7
	b.	Design voltage divider bias circuit to have $V_{CE} = V_E = 6V$ and $I_C = 1.5mA$ supply voltage is 24V and transistor $h_{fe} = 80$.	6
	c.	Determine the operating point of a Base bias Circuit using Silicon transistor with $\beta = 100$, $R_B = 500k\Omega$, $R_C = 2.5k\Omega$ and $V_{CC} = 20V$. Show the load line and Q- point.	7
MODULE - 3			
5	a.	Obtain an expression for the output voltage of an Subtractor using Op-amp	7
	b.	The input to the basic differentiator circuit is a sinusoidal voltage of peak value of 10	6

	c.	mV and frequency 1.5 kHz. Find the output if $R_f = 100 \text{ k}\Omega$ and $C_1 = 1\mu\text{F}$. Obtain an expression for the output voltage of an Inverting Summer using Op-amp	7
OR			
6	a.	Design an Inverting Schmitt Trigger using Op-Amp with $UTP = +4\text{V}$, $LTP = -4\text{V}$ and $V_{cc} = 18\text{V}$	7
	b.	Explain zero crossing detector using Op-Amp and also Sketch the input and output waveforms.	7
	c.	Design an adder circuit using op-amp to obtain an output expression of $V_o = - [0.1V_1 + 0.5V_2 + 20V_3]$, where V_1 , V_2 and V_3 are inputs. Select $R_f = 150 \text{ k}\Omega$.	6
MODULE - 4			
7	a.	Reduce the Boolean Expression and Implement using Universal gates $Y = \Sigma(1,2,4,7)$.	6
	b.	Deduce a Full Subtractor using Logic gates and write the truth table and logical expressions.	7
	c.	Explain the working of a JK flip-flop with logic diagram and truth table.	7
OR			
8	a.	Perform 1's and 2's Complement Subtraction for $(32)_{10} - (46)_{10}$	6
	b.	Implement Half adder using NAND gates.	7
	c.	Explain the working of an SR- latch using NOR gates.	7
MODULE - 5			
9	a.	Explain the various technology generations used in Wireless Communication System.	7
	b.	What is modulation and explain the need for modulation.	6
	c.	A modulating signal $10 \sin(2\pi \times 10^3 t)$ is used to modulate a carrier signal $20 \sin(2\pi \times 10^4 t)$. Find the modulation index, percentage of modulation and bandwidth of the modulated signal.	7
OR			
10	a.	Explain the basic principle of cellular communication.	7
	b.	Discuss different types of Electronic Communication.	7
	c.	A 500 Watts, 1MHz carrier is amplitude modulated with a sinusoidal signal of 1kHz. The depth of modulation is 60%. Calculate the band width, power in the side bands and the total power transmitted.	6